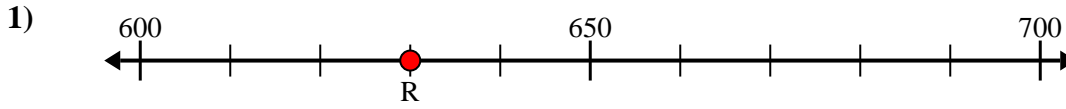





Find the value of R.


Answers




1. _____

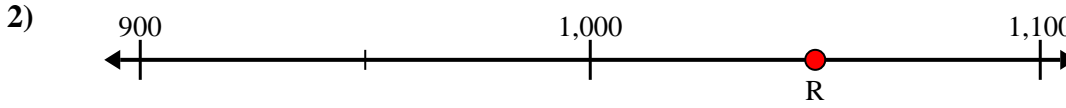


2. _____

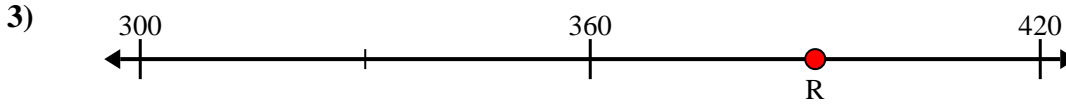


3. _____

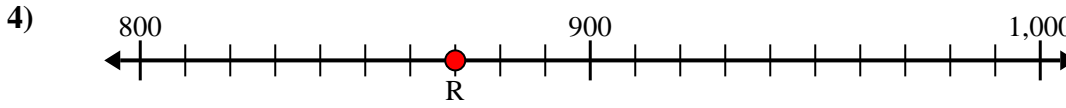


4. _____

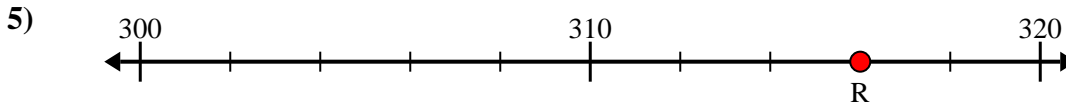


5. _____

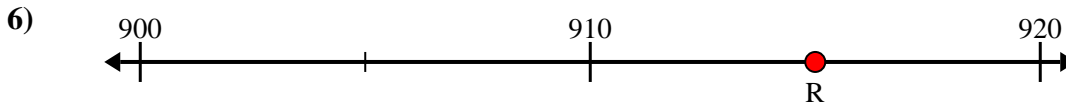


6. _____

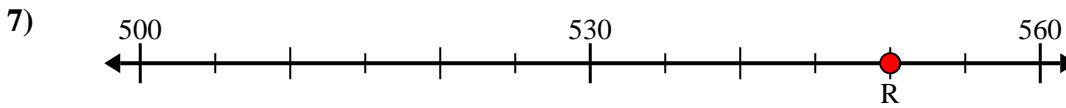


7. _____

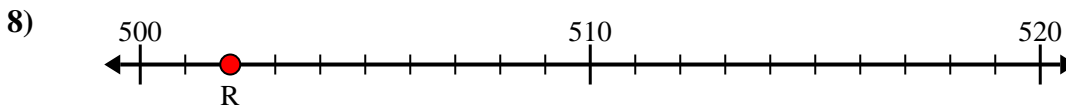

8. _____

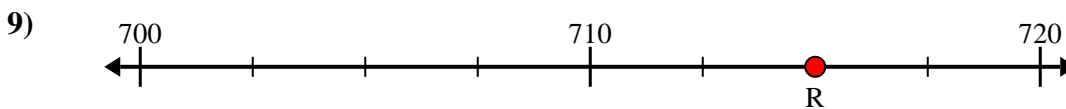











9. _____

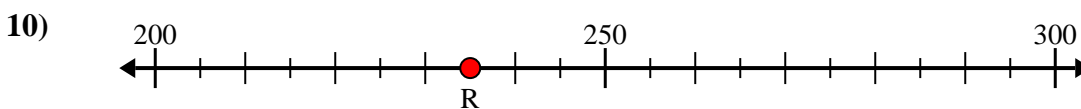

10. _____



Find the value of R.

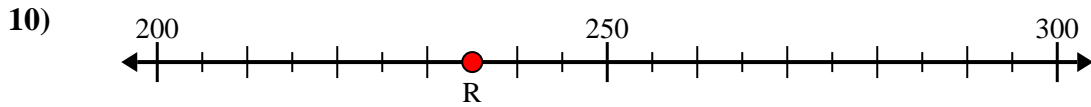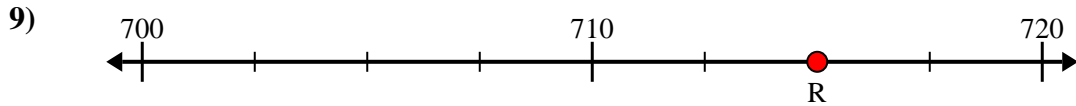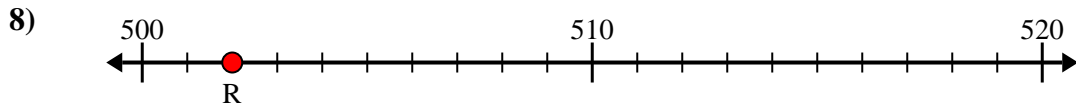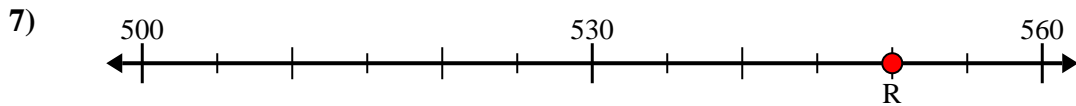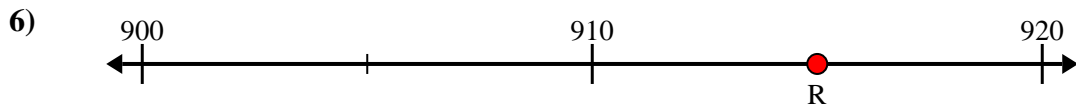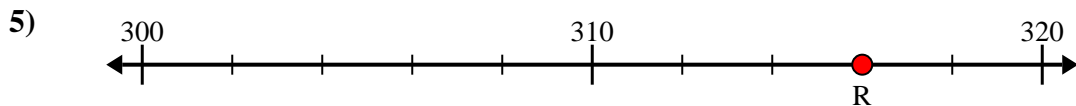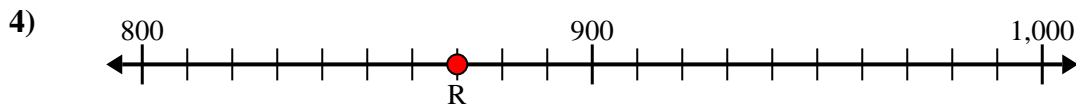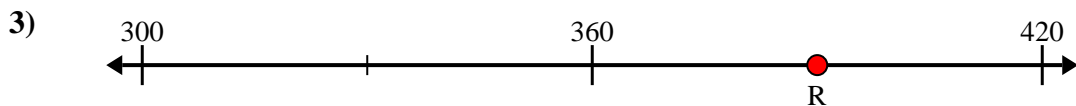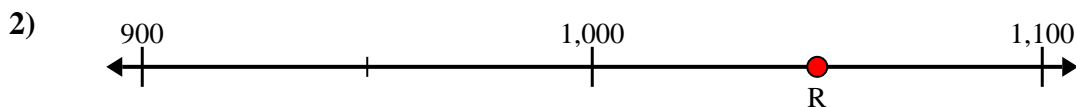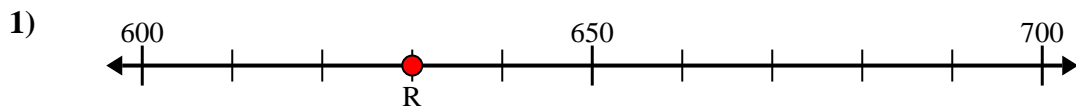

Answers

1. 630

2. 1,050

3. 390

4. 870

5. 316

6. 915

7. 550

8. 502

9. 715

10. 235