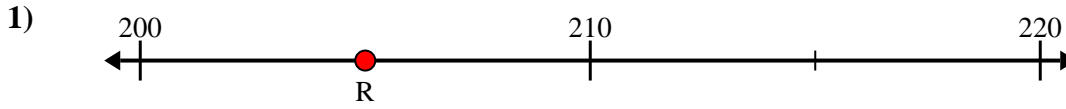





Find the value of R.


Answers




1. \_\_\_\_\_

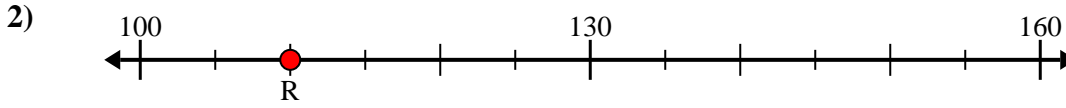


2. \_\_\_\_\_

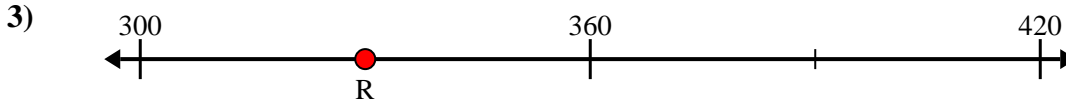


3. \_\_\_\_\_

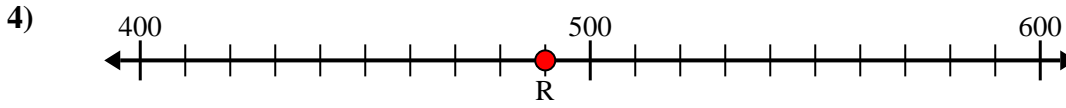


4. \_\_\_\_\_

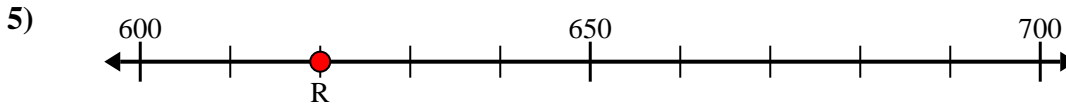


5. \_\_\_\_\_

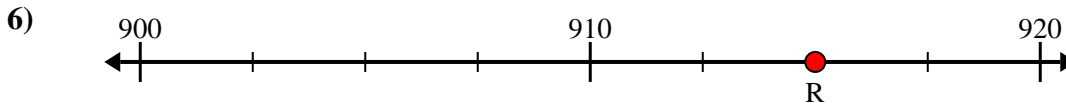


6. \_\_\_\_\_

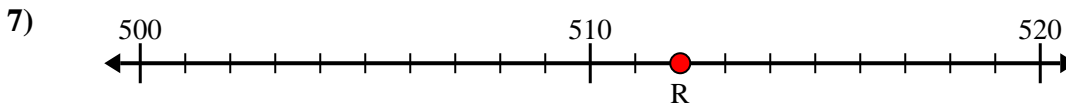


7. \_\_\_\_\_

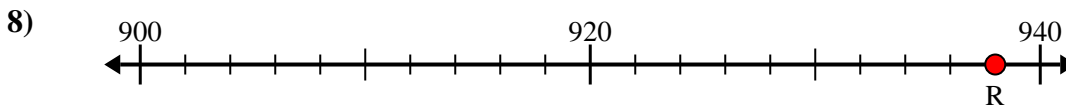

8. \_\_\_\_\_

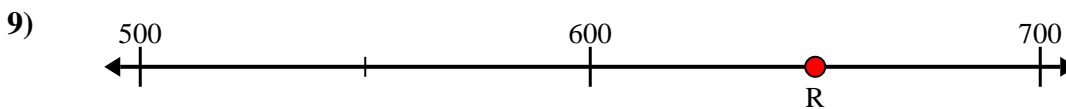











9. \_\_\_\_\_

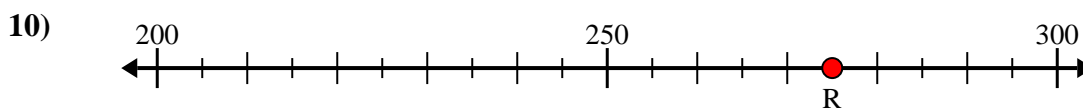

10. \_\_\_\_\_



Find the value of R.

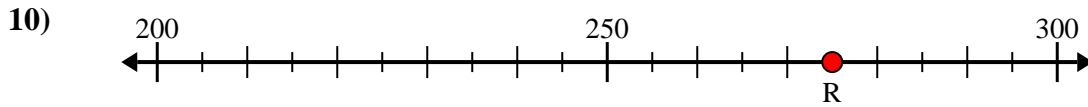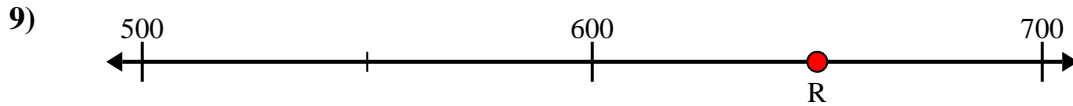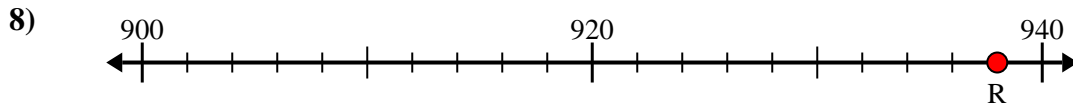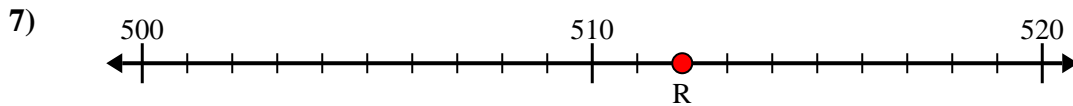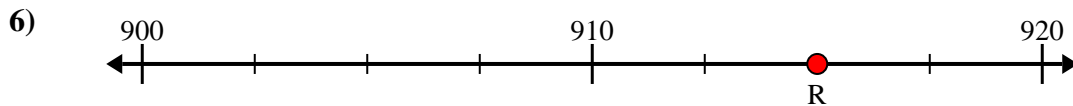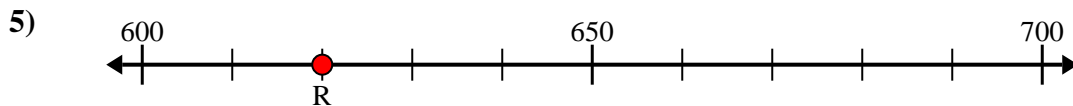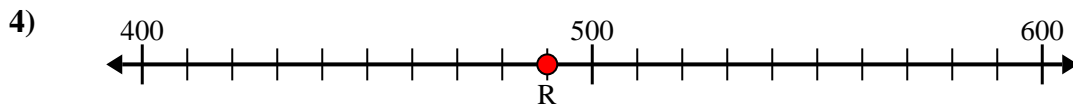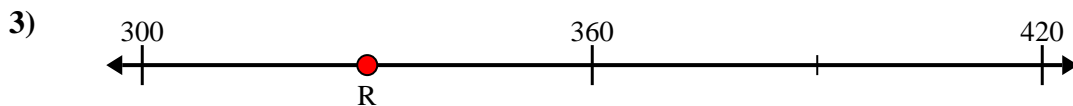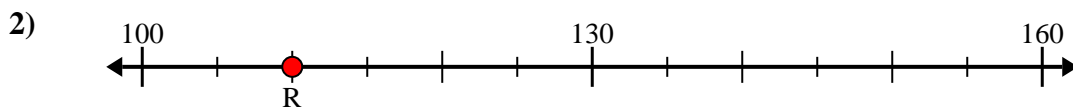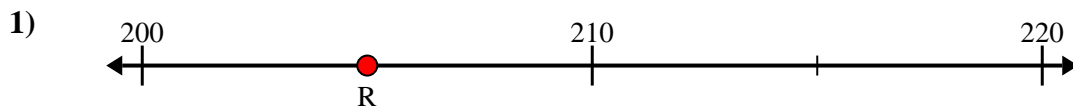

Answers

1. 205

2. 110

3. 330

4. 490

5. 620

6. 915

7. 512

8. 938

9. 650

10. 275