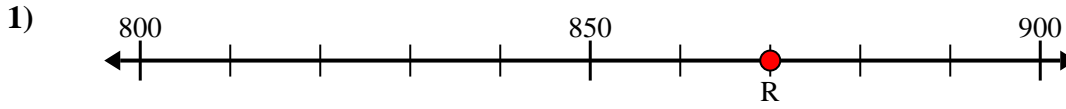





Find the value of R.


Answers




1. _____

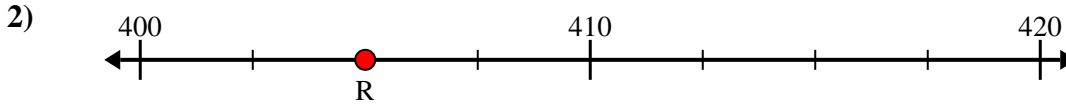


2. _____

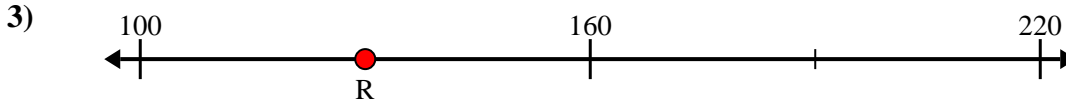

3. _____

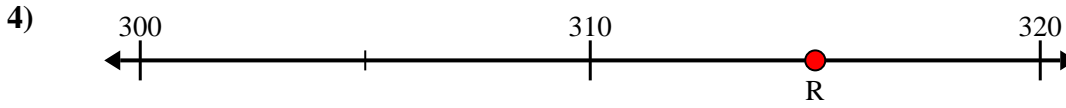


4. _____

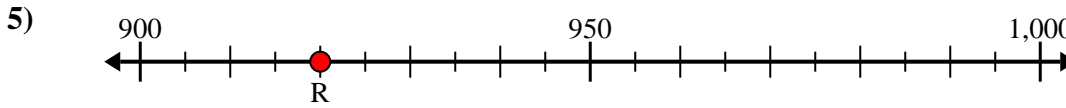


5. _____




6. _____

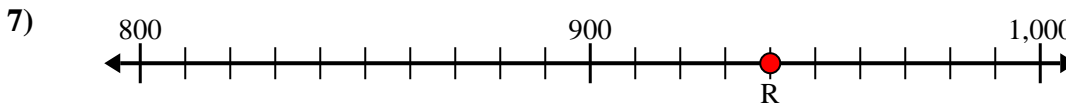


7. _____

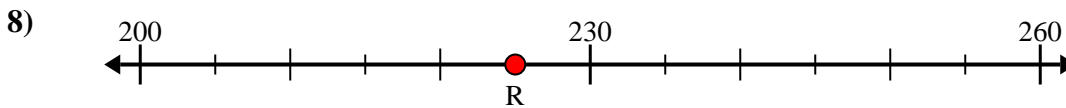

8. _____

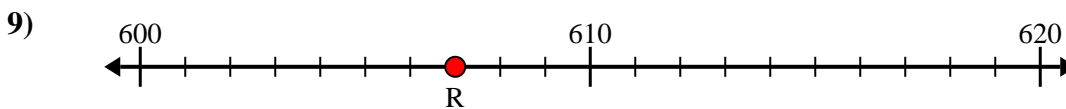











9. _____

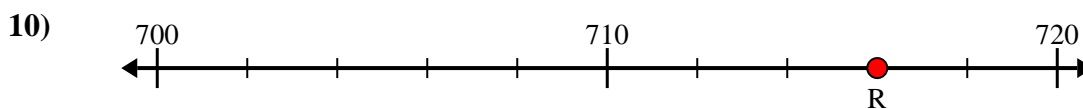

10. _____



Find the value of R.

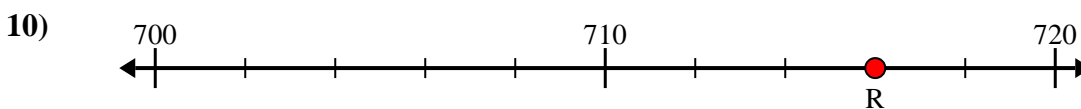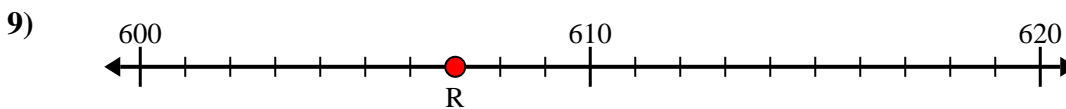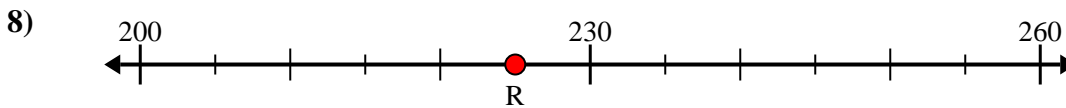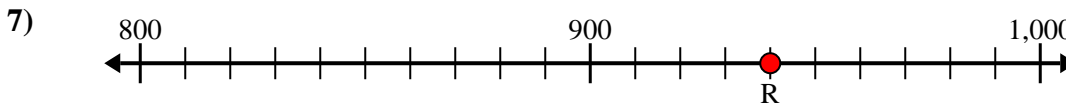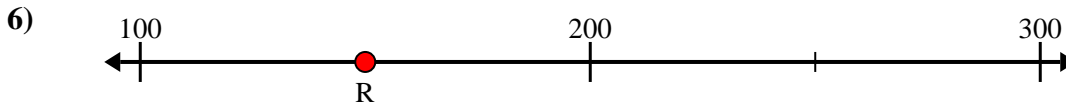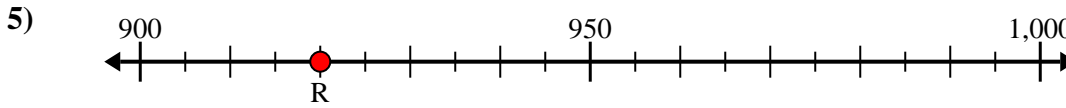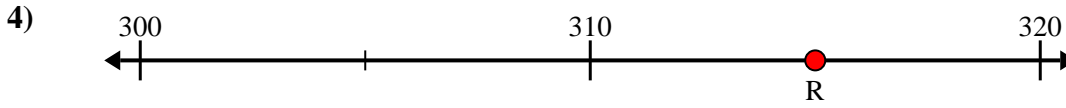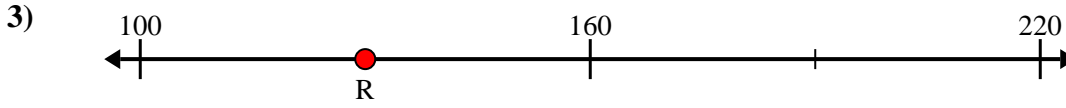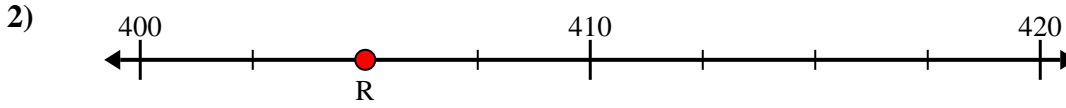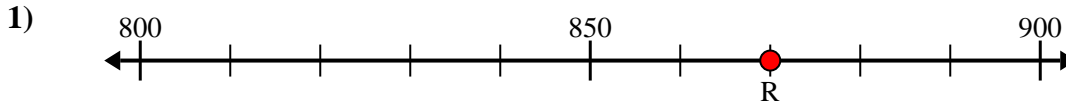

Answers

1. 870

2. 405

3. 130

4. 315

5. 920

6. 150

7. 940

8. 225

9. 607

10. 716