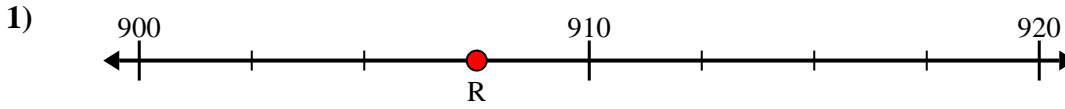





Find the value of R.


Answers




1. _____

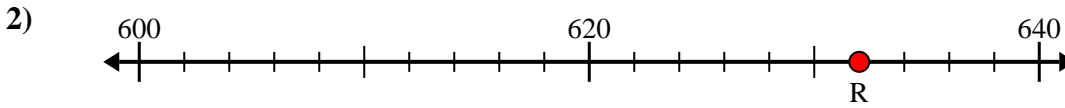


2. _____

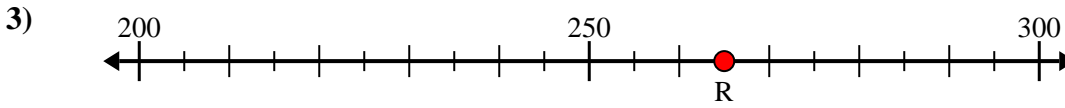


3. _____

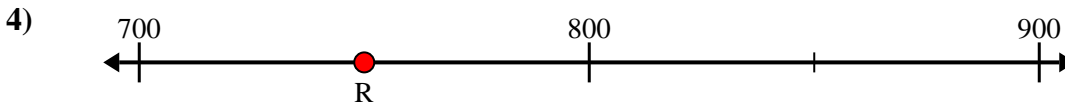


4. _____

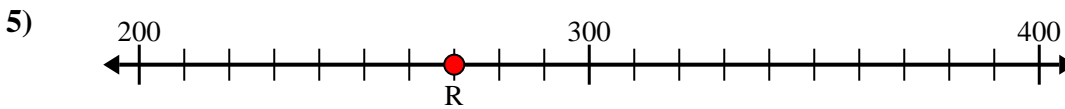


5. _____

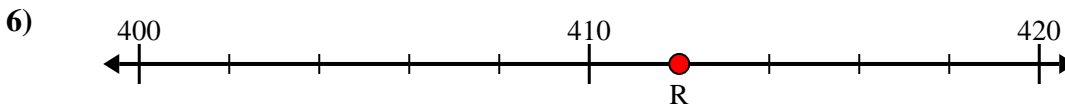


6. _____

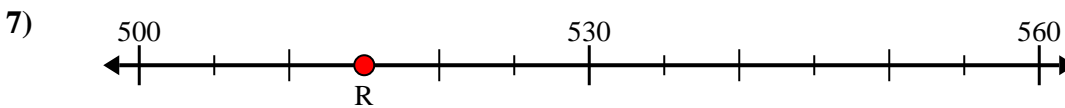


7. _____

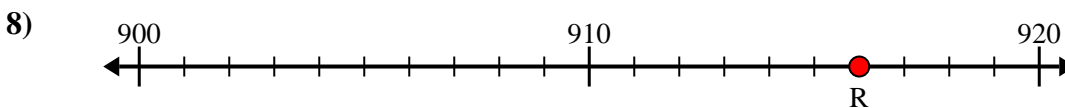

8. _____

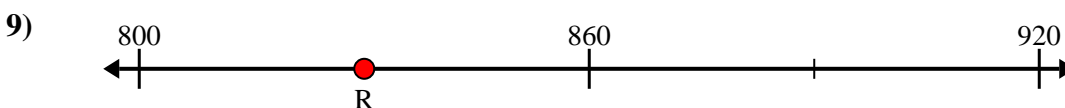











9. _____

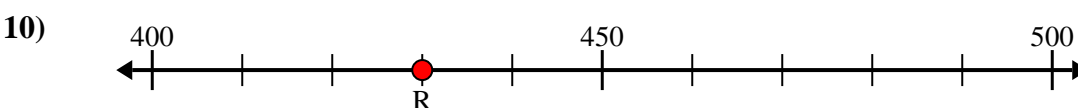

10. _____



Find the value of R.

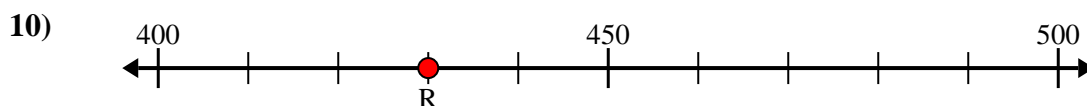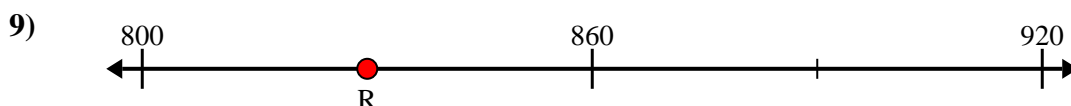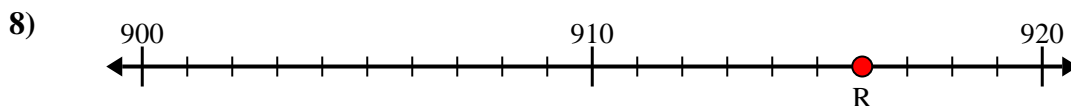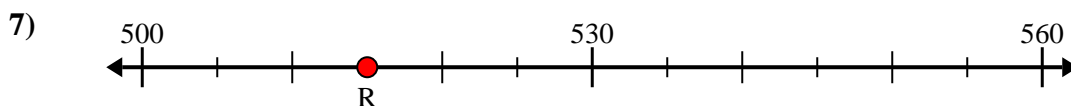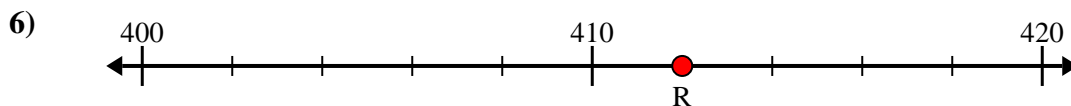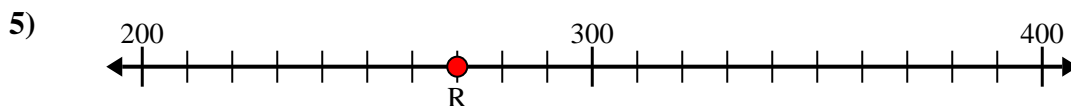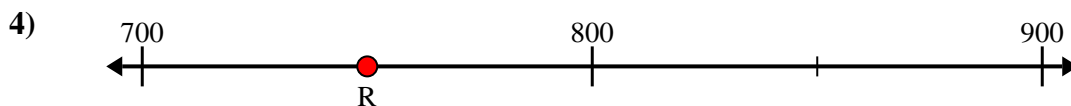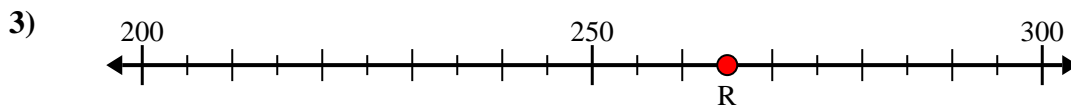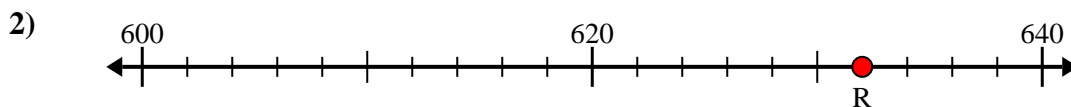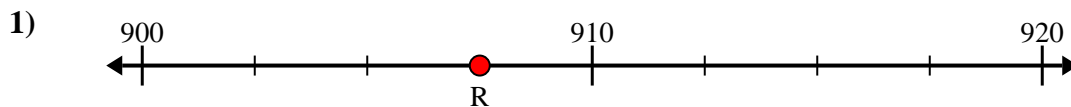Answers1. 907.52. 6323. 2654. 7505. 2706. 4127. 5158. 9169. 83010. 430