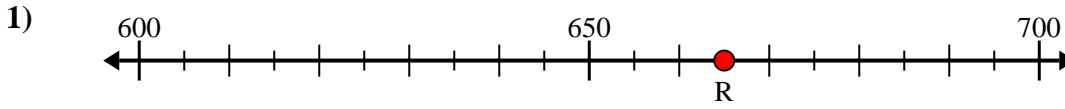





Find the value of R.


Answers




1. _____

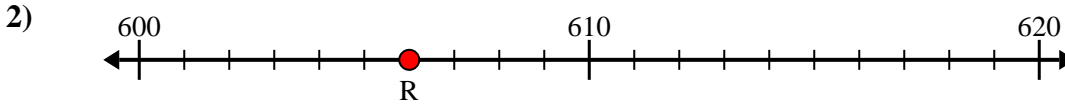


2. _____

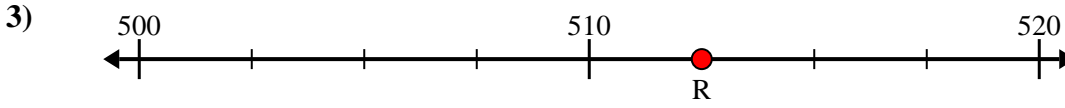

3. _____

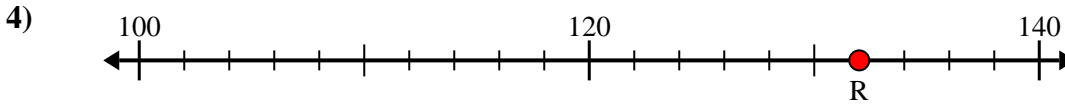


4. _____

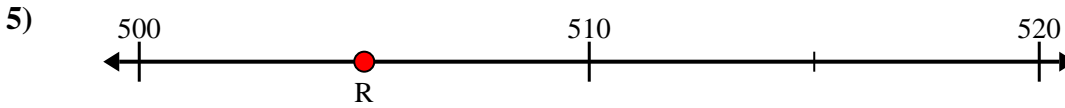


5. _____




6. _____

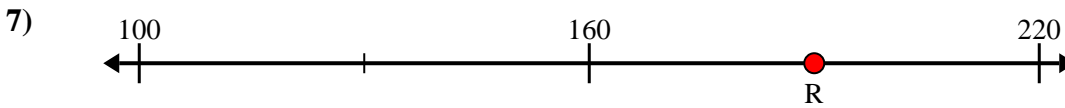


7. _____

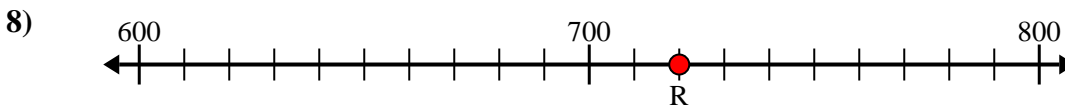

8. _____

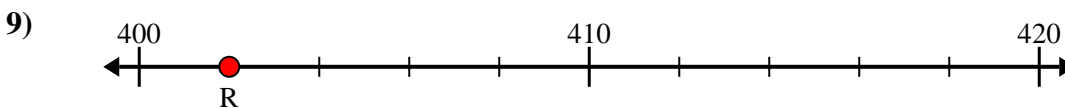











9. _____

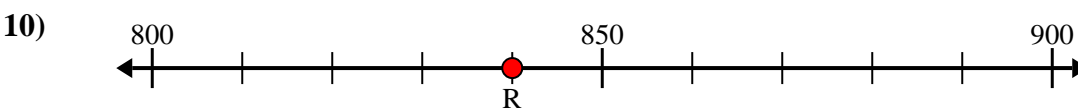

10. _____



Find the value of R.

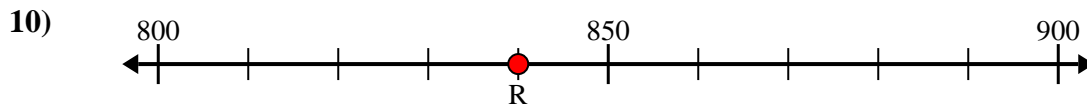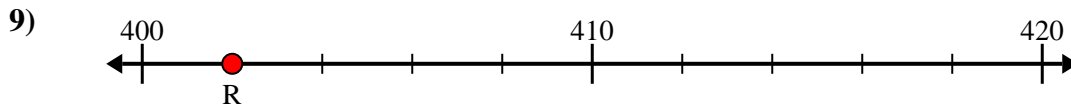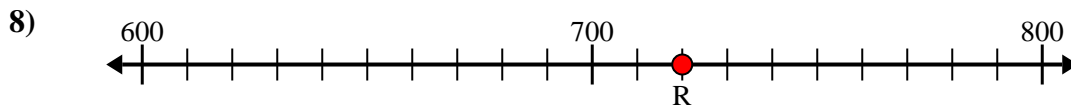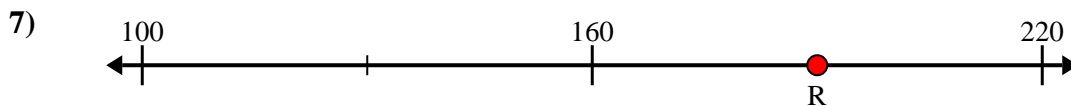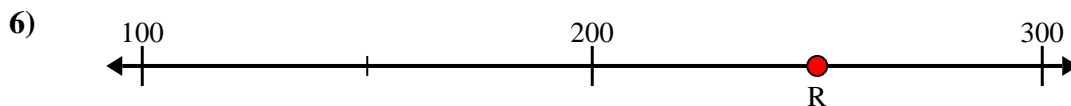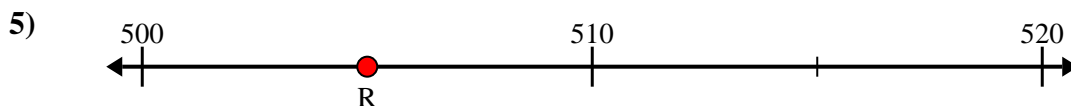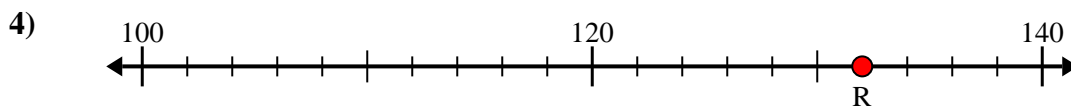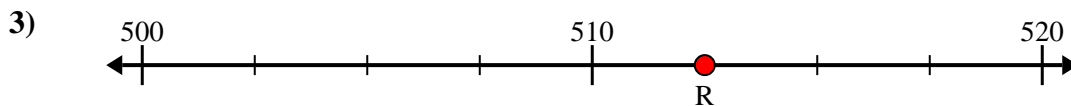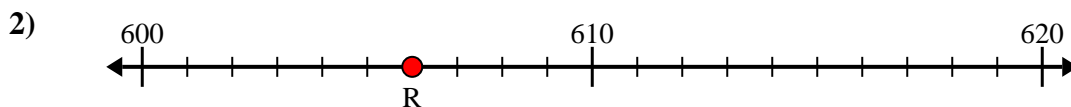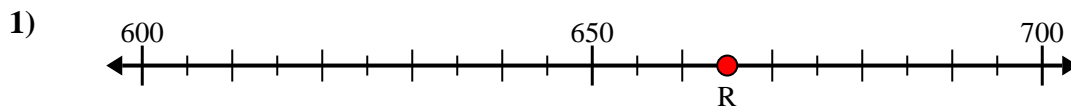**Answers**1. 6652. 6063. 512.54. 1325. 5056. 2507. 1908. 7209. 40210. 840