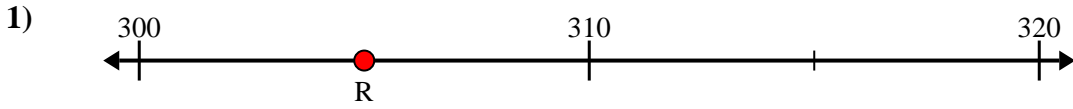





Find the value of R.


Answers




1. _____

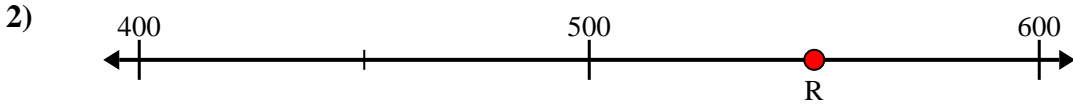


2. _____

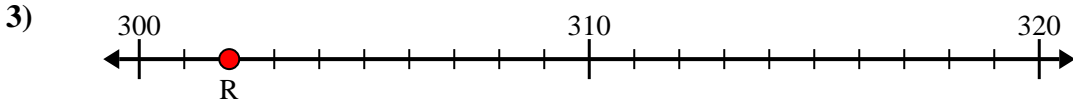


3. _____

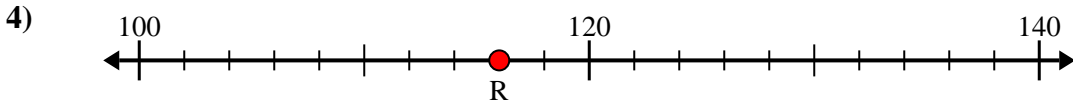


4. _____

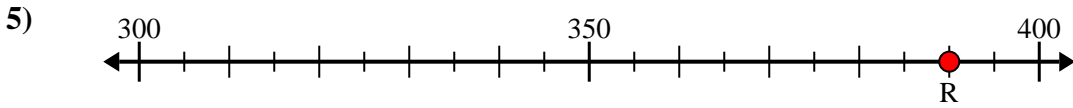


5. _____

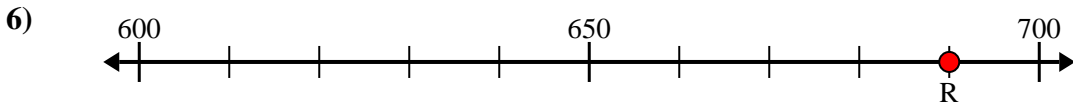


6. _____

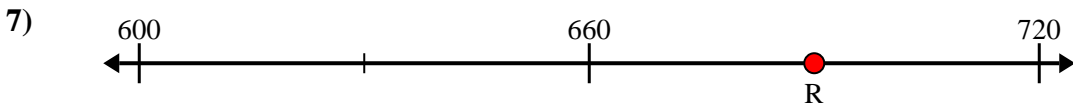


7. _____

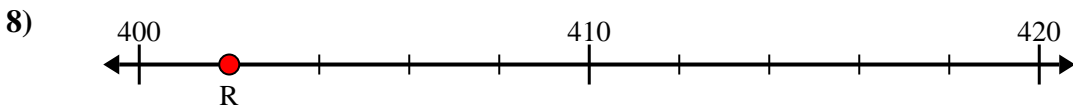

8. _____

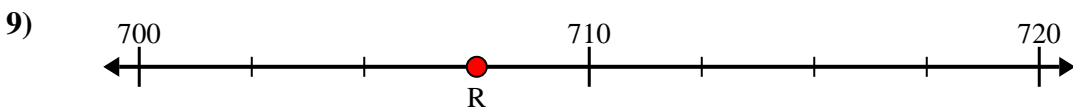











9. _____

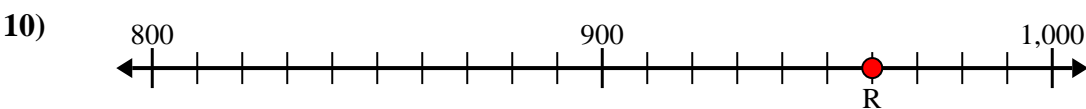

10. _____



Find the value of R.

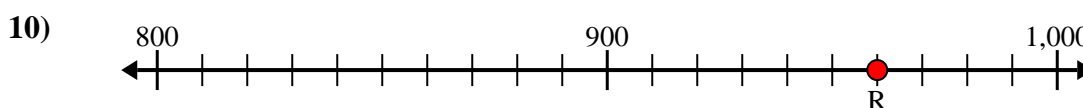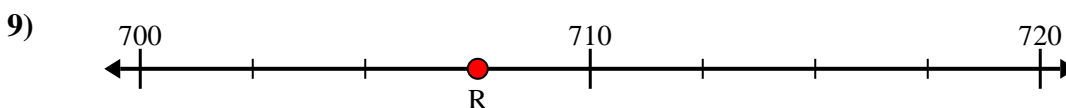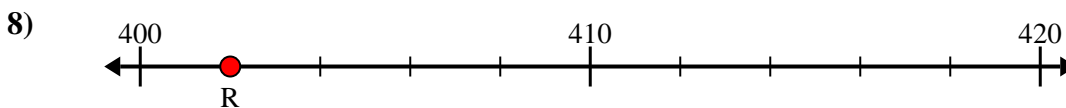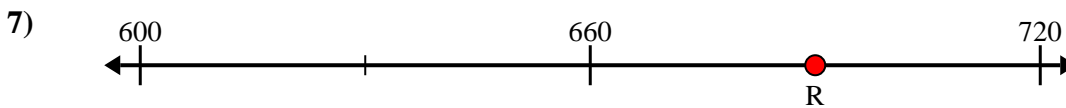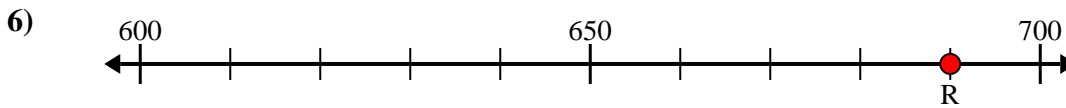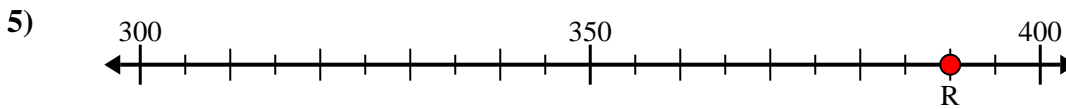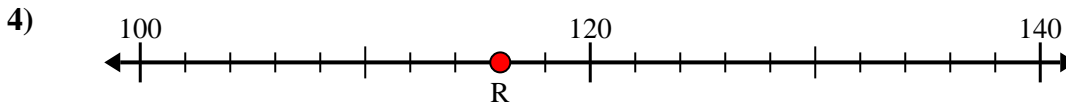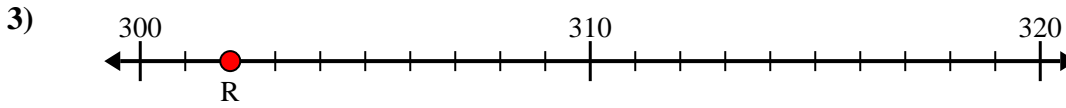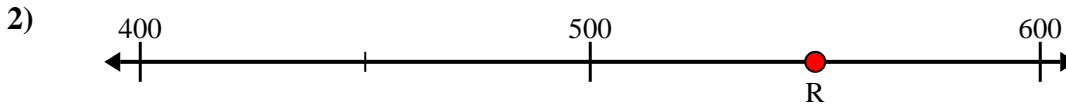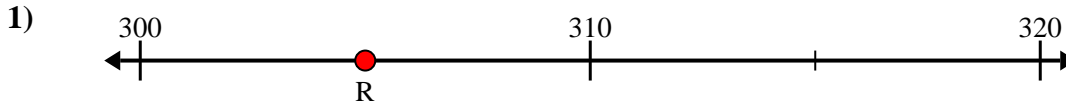

Answers

1. 305

2. 550

3. 302

4. 116

5. 390

6. 690

7. 690

8. 402

9. 707.5

10. 960